

NEWTON C. BRAGA

Robotics, Mechatronics, and Artificial Intelligence

Experimental Circuit
Blocks for Designers



Robotics, Mechatronics, and Artificial Intelligence

Experimental Projects

Other Books of Interest by Newnes

ELECTRONIC CIRCUIT INVESTIGATOR SERIES

ROBERT J. DAVIS, *Digital and Computer Projects*

NEWTON C. BRAGA, *CMOS Projects and Experiments: Fun with the 4093 Integrated Circuit*

NEWTON C. BRAGA, *Electronic Projects from the Next Dimension: Paranormal Experiments for Hobbyists*

NEWTON C. BRAGA, *Pirate Radio and Video: Experimental Transmitter Projects*

RELATED TITLES

ANDREW SINGMIN, *Beginning Electronics through Projects*

ANDREW SINGMIN, *Practical Audio Amplifier Circuit Projects*

ANDREW SINGMIN, *Beginning Digital Electronics through Projects*

Robotics, Mechatronics, and Artificial Intelligence

Experimental Projects

Newton C. Braga



Newnes

Boston Oxford Auckland Johannesburg Melbourne New Delhi

Newnes is an imprint of Butterworth–Heinemann.

Copyright © 2001 by Butterworth–Heinemann

 A member of the Reed Elsevier group

All rights reserved.

Although great care has been taken in the description of devices and experiments, the author wishes to alert readers to the dangers of using them without proper installation and due caution. Anyone making use of this information assumes all risk and liability arising from such use.

No part of this publication may be reproduced, stored in a retrieval system, or transmitted in any form or by any means, electronic, mechanical, photocopying, recording, or otherwise, without the prior written permission of the publisher.



Recognizing the importance of preserving what has been written, Butterworth–Heinemann prints its books on acid-free paper whenever possible.



Butterworth–Heinemann supports the efforts of American Forests and the Global ReLeaf program in its campaign for the betterment of trees, forests, and our environment.

ISBN 0-????-????-?

British Library Cataloguing-in-Publication Data

A catalogue record for this book is available from the British Library.

The publisher offers special discounts on bulk orders of this book.

For information, please contact:

Manager of Special Sales
Butterworth–Heinemann
225 Wildwood Avenue
Woburn, MA 01801-2041
Tel: 781-904-2500
Fax: 781-904-2620

For information on all Newnes publications available, contact our World Wide Web home page at:
<http://www.newnespress.com>

Transferred to Digital Printing in 2011

Contents

Acknowledgments xvii

About the Author xix

Chapter 1	Fundamentals of Robotics and Mechatronics	1
1.1	Purpose	1
1.2	History	1
1.3	The Structure of Robotics and Mechatronics Projects	3
1.3.1	Control	4
1.3.2	Actuators	4
1.4	Using Basic Blocks in Projects	9
1.5	Suggested Projects	9
1.6	Additional Information	14
1.7	Review Questions	15
Chapter 2	Motion Controls	17
2.1	Purpose	17
2.2	Theory	17
2.2.1	Direction	17
2.2.2	Speed	17
2.3	Characteristics	18
2.3.1	Voltage	18
2.3.2	Current	18
2.3.3	Power	18
2.3.4	Speed	19
2.4	Basic Blocks	19
	<i>Block 1:</i> Simple DC Control	22
	<i>Block 2:</i> Reversing the Direction	22
	<i>Block 3:</i> Two-Way Control	22
	<i>Block 4:</i> Controlling Two Motors with One Switch (I)	23
	<i>Block 5:</i> Controlling Two Motors with One Switch (II)	23
	<i>Block 6:</i> Half-Wave Rectifier	24
	<i>Block 7:</i> Full-Wave Control	24
	<i>Block 8:</i> Two-Speed Block Using Diodes	25
	<i>Block 9:</i> Multi-speed Control Using Diodes	25
	<i>Block 10:</i> Two-Speed Voltage Change from the Source	26
	<i>Block 11:</i> Power Booster	26
	<i>Block 12:</i> Multi-step Power Booster	27
	<i>Block 13:</i> Adding Inertia	27

<i>Block 14:</i>	Series–Parallel Switch	28
<i>Block 15:</i>	Motors in Series and Parallel	29
<i>Block 16:</i>	LED Direction Indicator	29
<i>Block 17:</i>	Current Indicator	30
<i>Block 18:</i>	Adding Sound (I)	30
<i>Block 19:</i>	Adding Sound (II)	31
<i>Block 20:</i>	Two-Wire × Two-Motor Control	32
2.5	Suggested Projects	32
2.6	Additional Information	32
2.7	Review Questions	33
Chapter 3 Controlling Motors, Relays, and Solenoids with Transistors		35
3.1	Purpose	35
3.2	Theory	35
3.2.1	The Relay	35
3.2.2	Basic Blocks Using Relays	36
<i>Block 21:</i>	Turning a Load On or Off	37
<i>Block 22:</i>	Current Reversion	37
<i>Block 23:</i>	Series–Parallel Switching (I)	37
<i>Block 24:</i>	Series–Parallel Switching (II)	38
<i>Block 25:</i>	Timed Relay	39
<i>Block 26:</i>	Short-Action Relay	39
<i>Block 27:</i>	Flasher	40
<i>Block 28:</i>	Passive Buzzer	40
<i>Block 29:</i>	Locked Relay	41
3.3	The Transistor as a Switch	41
3.3.1	Bipolar Transistors	41
3.3.2	Field Effect Transistor or FETs	43
3.4	Practical Blocks	44
<i>Block 30:</i>	Switching with an NPN Transistor	44
<i>Block 31:</i>	Switching with a PNP Transistor	45
<i>Block 32:</i>	Using an NPN Darlington Pair	45
<i>Block 33:</i>	Using a PNP Darlington Pair	46
<i>Block 34:</i>	Using a Darlington NPN Transistor	46
<i>Block 35:</i>	Using a Darlington PNP Transistor	47
<i>Block 36:</i>	Complementary Driver (I)	47
<i>Block 37:</i>	Complementary Driver (II)	47
<i>Block 38:</i>	Power FET Driver	48
3.5	More Blocks Using Relays and Transistors	48
<i>Block 39:</i>	Delayed Relay	49
<i>Block 40:</i>	Timed Relay	49
<i>Block 41:</i>	Long-Interval Delayed Relay	49
<i>Block 42:</i>	Long-Interval Timed Relay	50
<i>Block 43:</i>	Delayed Relay Using Power FET	50
<i>Block 44:</i>	Holding Circuit	51
3.5.1	Working with the Blocks	52
<i>Block 45:</i>	Reversing a Motor for a Few Seconds	52

<i>Block 46:</i>	Reversing and Stopping a Motor	53
<i>Block 47:</i>	Reversing a Motor and Reducing Its Speed	54
3.6	Suggested Projects	54
3.7	Additional Information	54
3.7.1	Information about Relays	54
3.7.2	Information about Transistors	56
3.8	Review Questions	57
Chapter 4	H-Bridges	59
4.1	Purpose	59
4.2	Theory	59
4.2.1	Half Bridge	59
4.2.2	H-Bridge or Full Bridge	60
4.3	Practical Circuits	62
<i>Block 48:</i>	Simple Half Bridge Using Symmetric Supply	63
<i>Block 49:</i>	Half Bridge Using Darlington Transistors	64
<i>Block 50:</i>	Full Bridge Using Complementary Bipolar Transistors	65
<i>Block 51:</i>	Full H-Bridge with Feedback	66
<i>Block 52:</i>	Full Bridge Using NPN Transistors	66
<i>Block 53:</i>	Full Bridge Using NPN Darlington Transistors	67
<i>Block 54:</i>	Full Bridge with Logic Control	68
<i>Block 55:</i>	Full Bridge with Logic Control and External Enable	69
<i>Block 56:</i>	Power MOSFET H-Bridge	69
<i>Block 57:</i>	H-Bridge Using Power MOSFETs with Enable	70
<i>Block 58:</i>	Combined Bipolar + MOSFET H-Bridge	71
<i>Block 59:</i>	Combined Darlington + Power MOSFET H-Bridge	72
<i>Block 60:</i>	R-S Flip-Flop H-Bridge	72
<i>Block 61:</i>	Complete H-Bridge	72
4.4	Integrated H-Bridges	74
<i>Block 62:</i>	H-Bridge Using the LMD18200	74
<i>Block 63:</i>	H-Bridge Using the LM18201	76
4.5	Additional Information	76
4.6	Special Recommendations	78
4.6.1	Decoupling Capacitors	78
4.6.2	Transistor Protection	79
4.6.3	Current Sensing	80
4.6.4	Fuses	80
4.7	Suggested Projects	80
4.8	Review Questions	81
Chapter 5	Linear and PWM Power Controls	83
5.1	Purpose	83
5.2	Theory	83
5.2.1	Two Types of Controls	84
5.2.2	Linear Controls	84
5.2.3	Pulse Width Modulation	84
5.2.4	Two Forms of PWM Controls	86
5.3	Basic Blocks	87

5.3.1	Linear Controls	87
	<i>Block 64:</i> Electronic Rheostat	88
	<i>Block 65:</i> Linear Control Using a Darlington Transistor	88
	<i>Block 66:</i> Linear Power Control Using a Zener Diode	89
5.3.2	Constant Current Sources	90
	<i>Block 67:</i> Constant Current Source Using Transistor	90
	<i>Block 68:</i> Constant Current Source Using the LM350T (3 A)	91
	<i>Block 69:</i> Variable Constant Current Source Using the LM338 (5 A)	92
5.3.3	PWM Blocks	92
	<i>Block 70:</i> PWM Basic Control Using the 4093 CMOS IC	92
	<i>Block 71:</i> PWM Control Using the 4001/4011 CMOS IC	92
	<i>Block 72:</i> Medium/High-Power PWM Control Using the 555 IC	94
	<i>Block 73:</i> Medium-Power PWM Using the 555 IC and a PNP Transistor	94
	<i>Block 74:</i> Anti-phase PWM Power Control Using the 555 IC	94
	<i>Block 75:</i> Power Anti-phase PWM Control Using the 555 IC	96
	<i>Block 76:</i> PWM Control Using the LM350	96
5.4	Additional Information	97
5.5	Suggested Projects	98
5.6	Review Questions	98
Chapter 6 Power Control Using Thyristors		99
6.1	Purpose	99
6.2	Theory	99
	6.2.1 Silicon Controlled Rectifiers	99
	6.2.2 Triacs	101
	6.2.3 Other Devices of the Thyristor Family	102
6.3	Basic Blocks Using SCRs	105
	<i>Block 77:</i> Turning a Load On and Off with an SCR	105
	<i>Block 78:</i> Delayed Turn-On Switch with SCR	106
	<i>Block 79:</i> Touch Switch Using an SCR	106
	<i>Block 80:</i> Triggering an SCR with Positive Pulses	107
	<i>Block 81:</i> Triggering SCRs with Negative Pulses	107
	<i>Block 82:</i> Crowbar Protection	107
	<i>Block 83:</i> Overcurrent Protection	109
	<i>Block 84:</i> R-S Flip-Flop Using an SCR	109
6.3.1	SCRs in AC Circuits	110
	<i>Block 85:</i> Simple AC Switch	110
	<i>Block 86:</i> Full-Wave AC Switch (I)	110
	<i>Block 87:</i> Full-Wave AC Switch (II)	111
	<i>Block 88:</i> Dimmer and Speed Control	111
	<i>Block 89:</i> Full-Wave Dimmer	113
	<i>Block 90:</i> Dimmer Using UJT and SCR	113
6.3.2	Blocks Using Triacs	114
	<i>Block 91:</i> High-Power AC Switch	114
	<i>Block 92:</i> High-Power Dimmer	114
6.4	Additional Information	115
	6.4.1 Care when Using Inductive Loads	115

6.4.2	Characteristics of Some Common SCRs and Triacs	115
6.5	Suggested Projects	116
6.6	Review Questions	116
Chapter 7	Solenoids, Servomotors, and Shape Memory Alloys	119
7.1	Purpose	119
7.2	Theory	119
7.2.1	Shape Memory Alloys	119
7.2.2	The Solenoid	121
7.2.3	The Servomotor	122
7.3	Practical Blocks	124
7.3.1	Blocks for Electronic Muscles (SMAs)	124
	<i>Block 93:</i> Simple Drive Circuit for SMAs	124
	<i>Block 94:</i> Rheostat for SMA	125
	<i>Block 95:</i> Constant Current Source	125
	<i>Block 96:</i> NPN Transistor Drive for SMA	126
	<i>Block 97:</i> Using a Bipolar PNP transistor	126
	<i>Block 98:</i> Driving SMA from Power MOSFETs	126
7.3.2	Blocks for Solenoids	127
	<i>Block 99:</i> Turning a Solenoid On and Off	127
	<i>Block 100:</i> Determining the Force of a Solenoid	127
	<i>Block 101:</i> Intelligent Control for Two Solenoids	128
	<i>Block 102:</i> Intelligent Solenoid Control Using Darlington Transistors	129
	<i>Block 103:</i> Intelligent Control Using CMOS Logic	130
	<i>Block 104:</i> Intelligent Circuit Using CMOS IC and Power CMOS	130
	<i>Block 105:</i> Current Sensing (I)	130
	<i>Block 106:</i> Current Sensing (II)	131
7.3.3	Blocks for Servos	133
	<i>Block 107:</i> Servo Control Using DC Motors	133
	<i>Block 108:</i> Control for R/C Standard Servos	134
7.4	Additional Information	134
7.5	Suggested Projects	134
7.6	Review Questions	135
Chapter 8	Stepper Motors	137
8.1	Purpose	137
8.2	Theory	137
8.2.1	How It Works	138
8.3	How to Use Stepper Motors	140
8.3.1	Voltage and Current	140
8.3.2	Sequence	141
8.3.3	Step Angle	141
8.3.4	Pulse Rate	141
8.3.5	Torque	142
8.3.6	Braking Effect	142
8.4	Blocks Using Stepper Motors	142
	<i>Block 109:</i> Standard Block Using Bipolar NPN Transistors	142
	<i>Block 110:</i> Standard Block Using Darlington NPN Transistors	142

<i>Block 111:</i> Driving a Stepper Motor with PNP Transistors	143
<i>Block 112:</i> Using PNP Darlington Transistors	144
<i>Block 113:</i> Driving a Stepper Motor with Power MOSFETs	145
<i>Block 114:</i> Step Generator Using the 555 IC	145
<i>Block 115:</i> Step Generator Using the 4093 IC	146
<i>Block 116:</i> Step-by-Step Generator.	147
<i>Block 117:</i> Control for Two-Phase Stepper Motor	147
8.4.1 Using ICs	147
<i>Block 118:</i> Driving a Stepper Motor with the ULN2002 and ULN2003	148
<i>Block 119:</i> Driving Stepper Motors with the MC1413/MC1416	148
<i>Block 120:</i> Complete Stepper Motor Control with the SAA1027.	148
<i>Block 121:</i> Complete Stepper Motor Control Using the UCN4202	150
<i>Block 122:</i> LED Monitor for Stepper Motor Operation	151
8.5 Additional Information.	152
8.6 Suggested Projects	152
8.7 Review Questions.	153
Chapter 9 On-Off Sensors.	155
9.1 Purpose	155
9.2 Theory	155
9.2.1 Debouncing	157
9.2.2 Switches as Sensors	158
9.2.3 Reed Switches	158
9.2.4 Home-Made Sensors	159
9.2.5 Programmed or Sequential Mechanical Sensors	159
9.3 Basic Blocks Using Sensors.	159
<i>Block 123:</i> Turning a Load On	160
<i>Block 124:</i> Turning a Load Off.	160
<i>Block 125:</i> Contact Conditioner with a Capacitor.	160
<i>Block 126:</i> Low-Current Turn-On Sensor with Contact Conditioner	161
<i>Block 127:</i> Low-Current Turn-Off Sensor With Contact Conditioner	161
<i>Block 128:</i> Contact Conditioner Using the 555 IC	162
<i>Block 129:</i> Contact Conditioner Using the 4093 CMOS IC (I)	163
<i>Block 130:</i> Contact Conditioner Using the 4093 CMOS IC (II).	163
<i>Block 131:</i> TTL Contact Conditioner Using the 7400 IC	163
<i>Block 132:</i> Contact Conditioner for Two Sensors—Bistable	164
<i>Block 133:</i> Contact Conditioner for SPDT Sensor	164
<i>Block 134:</i> Contact Conditioner for Two Sensors.	165
9.3.1 Notes on Compatible Blocks	165
9.3.2 Controlling Motors and Loads	165
<i>Block 135:</i> Direction Control Using a Mechanical Sensor	165
<i>Block 136:</i> Controlling Two Loads.	166
<i>Block 137:</i> High-Low Sensor	166
<i>Block 138:</i> High-Power Motor Control.	166
<i>Block 139:</i> Timed Sensor Using a 555 IC.	167
<i>Block 140:</i> High-Current Control for Mechanical Sensors.	168
<i>Block 141:</i> Multi-voltage Control for Mechanical Sensors.	168

<i>Block 142: Priority Switch</i>	169
<i>Block 143: Tachometric Sensor</i>	170
<i>Block 144: Missing Pulse Detector</i>	170
9.4 Suggested Projects	171
9.5 Additional Information	171
9.6 Review Questions	173
Chapter 10 Resistive Sensors	175
10.1 Purpose	175
10.1.1 Theory	175
10.1.2 The LDR or CdS Cell	175
10.1.3 Negative Temperature Coefficient Resistors	176
10.1.4 Pressure Sensors	177
10.1.5 Potentiometers as Position Sensors	177
10.1.6 Touch Sensors	177
10.2 How to Use Resistive Sensors	178
10.3 Practical Blocks	179
<i>Block 145: Basic Resistive Sensor Circuit (I)</i>	179
<i>Block 146: Basic Resistive Sensor Circuit (II)</i>	179
<i>Block 147: Basic Block Using a PNP Transistor (I)</i>	179
<i>Block 148: Basic Block Using PNP Transistor (II)</i>	180
<i>Block 149: Differential Sensor</i>	180
<i>Block 150: Snap Action for Resistive Sensors (I)</i>	181
<i>Block 151: Snap Action for Resistive Sensors (II)</i>	182
<i>Block 152: Increasing Sensitivity</i>	182
<i>Block 153: Light-Activated Circuit Using an SCR</i>	183
<i>Block 154: Dark-Activated Circuit Using an SCR</i>	184
<i>Block 155: Priority Circuit Using Resistive Sensors</i>	184
<i>Block 156: Opto-Isolator Using LDR</i>	185
<i>Block 157: Opto-Isolator with Logic Input (TTL and CMOS)</i>	185
<i>Block 158: Current Sensor Using an NTC</i>	186
<i>Block 159: Thermal Crowbar</i>	187
<i>Block 160: Light/Temperature-Controlled Oscillator</i>	187
<i>Block 161: Light-Sensitive/Temperature-Dependent Oscillator</i>	187
<i>Block 162: Light/Temperature-Dependent Oscillator</i>	188
<i>Block 163: Light/Temperature-Triggered Monostable</i>	188
<i>Block 164: Fast Monostable Sensor</i>	189
<i>Block 165: Light/Temperature-Dependent Oscillator</i>	190
10.4 Additional Information	191
10.5 Suggested Projects	191
10.6 Review Questions	191
Chapter 11 Operational Amplifiers and Comparators	193
11.1 Purpose	193
11.2 Theory	193
11.2.1 Operational Amplifiers and Comparators	193
11.2.2 The Window Comparator	195
11.2.3 How to Use Operational Amplifiers and Comparators	196

11.2.4	Choosing an Opamp	197
11.2.5	Power Supplies	198
11.3	Practical Blocks	199
	<i>Block 166:</i> Voltage Follower	199
	<i>Block 167:</i> Amplifier with Gain	199
	<i>Block 168:</i> Driving an NPN transistor	200
	<i>Block 169:</i> Driving a PNP Transistor	201
	<i>Block 170:</i> Basic Voltage Comparator	201
	<i>Block 171:</i> Negative Voltage Comparator	202
	<i>Block 172:</i> Using Resistive Sensors (I)	202
	<i>Block 173:</i> Using Resistive Sensors (II)	203
	<i>Block 174:</i> Resistive Sensors Driving PNP Transistor	203
	<i>Block 175:</i> Differential Sensor	204
	<i>Block 176:</i> Touch Sensor/Pressure Sensor	205
	<i>Block 177:</i> Delayed Turn-On Relay	205
	<i>Block 178:</i> Driving TTL Blocks	206
	<i>Block 179:</i> Power Comparator	206
	<i>Block 180:</i> Low-Frequency Squarewave Oscillator	206
	<i>Block 181:</i> Double Comparator	207
	<i>Block 182:</i> Step Comparator	208
	<i>Block 183:</i> Window Comparator (I)	209
	<i>Block 184:</i> Window Comparator (II)	209
11.4	Additional Information	210
11.5	Suggested Projects	211
11.6	Review Questions	211
Chapter 12 Remote Controls and Remote Sensing		213
12.1	Purpose	213
12.2	Theory	213
	12.2.1 Wires	213
	12.2.2 Light	213
12.3	Infrared	214
	12.3.1 Sound	214
	12.3.2 Radio	215
	12.3.3 Electromagnetic Interference	215
12.4	Choice and Use of a Remote Control	216
12.5	Blocks	216
	<i>Block 185:</i> Remote Control Using Wires	216
	<i>Block 186:</i> Multi-wire Control	217
	<i>Block 187:</i> Sequential Control Using Wires	218
	<i>Block 188:</i> Matrix Control	219
	<i>Block 189:</i> Tone Generator	220
	<i>Block 190:</i> AC Switch (I)	221
	<i>Block 191:</i> AC Switch (II)	221
	<i>Block 192:</i> PLL Tone Decoder	222
	<i>Block 193:</i> Multi-tone Transmitter	223
	<i>Block 194:</i> Multichannel Tone Decoder	223

<i>Block 195:</i> Remote Control Using the AC Power Line, Transmitter	224
<i>Block 196:</i> Remote Control Using the AC Power Line, Receiver	224
<i>Block 197:</i> Flashlight Remote Control	225
<i>Block 198:</i> Infrared Transmitter	226
<i>Block 199:</i> Infrared Receiver	227
<i>Block 200:</i> Sound/Ultrasonic Transmitter	227
<i>Block 201:</i> Low-Impedance Sound/Ultrasonic Receiver	228
<i>Block 202:</i> Audible Receiver for Electret Microphone	228
<i>Block 203:</i> 30 to 100 MHz Transmitter Block	229
<i>Block 204:</i> Using a Small FM Radio as Remote Control Receiver	230
<i>Block 205:</i> 30 to 100 MHz Super-Regenerative Receiver	230
<i>Block 206:</i> Coder Using the MC145026	230
<i>Block 207:</i> Decoder Using the MC145026	230
Additional Information	232
Suggested Projects	232
12.6 Review Questions	234
Chapter 13 Logic Blocks	235
13.1 Purpose	235
13.2 Theory	235
13.2.1 Gates, Inverters, and Buffers	235
13.2.2 Monostable/Bistable	237
13.2.3 Counters and Decoders	238
13.2.4 Voltage-Controlled Oscillators	238
13.2.5 Memory	238
13.3 How to Use Logic Blocks	238
13.4 Blocks	239
<i>Block 208:</i> NOR Gate Using a Transistor	239
<i>Block 209:</i> NAND Gate Using a Transistor	239
<i>Block 210:</i> Logic Inverter Using a Transistor	240
<i>Block 211:</i> Basic Monostable Using the 555 IC	240
<i>Block 212:</i> Sequential Monostable	241
<i>Block 213:</i> Multi-timing Using the 555 IC	241
<i>Block 214:</i> Bistable Block	241
<i>Block 215:</i> Complete Bistable Using the 4013 IC	242
<i>Block 216:</i> Frequency Divider	243
<i>Block 217:</i> Frequency Divider Using the 4020 IC	244
<i>Block 218:</i> Divide-by-10 Counter Using the 4017 IC	244
<i>Block 219:</i> Divide-by-n Using the 4017 IC	245
<i>Block 220:</i> Programming with Diodes	246
<i>Block 221:</i> Digital-to-Analog Converter (DAC)	246
<i>Block 222:</i> Sequential Programming Using a Diode Matrix	247
<i>Block 223:</i> Voltage-Controlled Oscillator	247
<i>Block 224:</i> Logic Switch	249
<i>Block 225:</i> Diode Matrix	249
<i>Block 226:</i> R/2R Network—DAC	249
<i>Block 227:</i> Binary Coded Decimal Counter/Decoder	250

<i>Block 228: Complete DAC</i>	251
<i>Block 229: 64-Bit RAM</i>	251
13.5 Additional Information	253
13.6 Suggested Projects	254
13.7 Review Questions	255
Chapter 14 Intelligence and the Computer	257
14.1 Purpose	257
14.2 Theory	257
14.2.1 What is Intelligence?	257
14.2.2 Intelligence by Hardware and Software	258
14.2.3 Electronic Neurons and Neural Networks	258
14.2.4 Fuzzy Logic and Intelligent Software	259
14.2.5 Microcontrollers and Microprocessors	259
14.2.6 Personal Computers	260
14.3 Using the Hardware	260
14.4 Blocks	260
<i>Block 230: Learning Circuit Using Power MOSFET</i>	260
<i>Block 231: Learning Circuit Using an IC</i>	261
<i>Block 232: Sample-and-Hold Circuit</i>	261
<i>Block 233: High-Power Learning Circuit</i>	262
<i>Block 234: Light-Conditioned Circuit</i>	262
<i>Block 235: Thermal Memory</i>	263
<i>Block 236: Teachable Window Comparator</i>	264
<i>Block 237: Electronic Neuron (I)</i>	265
<i>Block 238: Electronic Neuron (II)</i>	265
<i>Block 239: Learning Circuit Using the 4017 IC</i>	266
<i>Block 240: Integrate-and-Fire Neuron Using Operational Amplifiers</i>	266
14.4.1 Connecting a Computer	267
<i>Block 241: Simplest Parallel Interface</i>	268
<i>Block 242: Parallel Interface (II)</i>	268
<i>Block 243: Isolated Interface (I)</i>	268
<i>Block 244: Isolated Interface (II)</i>	269
<i>Block 245: Interface for AC-Powered Loads</i>	269
<i>Block 246: Data Acquisition Interface Using Comparators</i>	270
<i>Block 247: Data Acquisition Interface Using the ADC0808</i>	270
14.5 Additional Information	271
14.6 Other Microcontrollers	272
14.7 Suggested Projects	272
14.8 Review Questions	272
Chapter 15 Other Blocks: Light and Sound Effects	273
15.1 Purpose	273
15.2 Theory	273
15.2.1 Light Effects	273
15.2.2 Sound Effects	274
15.2.3 Other Blocks	274
15.2.4 Self-Defense	275

15.2.5	Power Supplies	275
15.2.6	Battery Chargers	275
15.3	Blocks	275
	<i>Block 248:</i> Low-Voltage LED Flasher	276
	<i>Block 249:</i> Block 317–LED Lamp Flasher	276
	<i>Block 250:</i> Fluorescent Lamp Inverter	277
	<i>Block 251:</i> Fluorescent Lamp Flasher	278
	<i>Block 252:</i> LED Sequencer	278
	<i>Block 253:</i> Driving Incandescent Lamps	279
	<i>Block 254:</i> Bar/Dot Display Driver	280
	<i>Block 255:</i> Variable-Sound Siren	281
	<i>Block 256:</i> Dual-Tone Siren	281
	<i>Block 257:</i> Sound and Light	281
	<i>Block 258:</i> High-Voltage Defense	282
	<i>Block 259:</i> Solenoid Gun	283
	<i>Block 260:</i> Laser Gun	284
	<i>Block 261:</i> General-Purpose Power Supply	284
	<i>Block 262:</i> Battery Charger	285
15.4	Additional Information	286
	15.4.1 Musical Modules	286
	15.4.2 Other Circuits	287
15.5	Suggested Projects	287
15.6	Review Questions	288
Chapter 16 Working Safely		289
16.1	The Importance of Safety	289
16.2	Experimental and Industrial Robots	289
16.3	Safety Rules	291
Answers to Review Questions		293