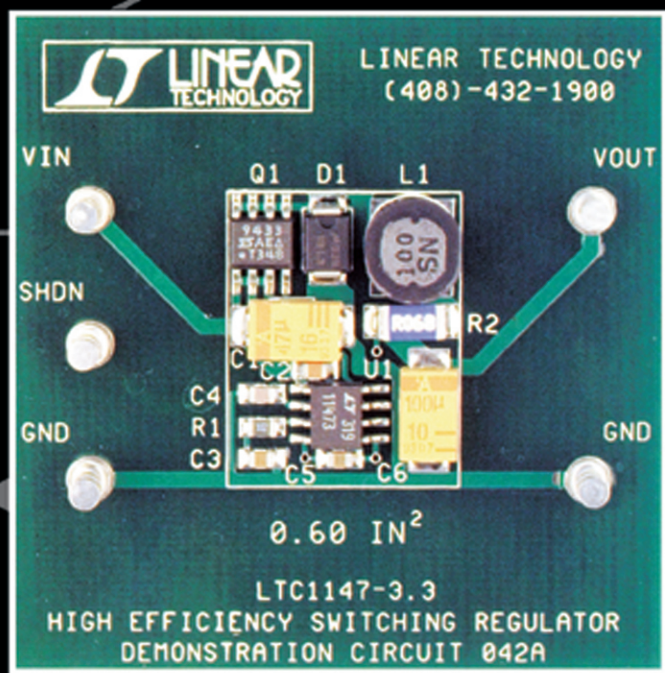


JOHN D. LENK

SIMPLIFIED DESIGN OF SWITCHING POWER SUPPLIES



Simplified Design of Switching Power Supplies

The EDN Series for Design Engineers

J. Lenk *Simplified Design of Switching Power Supplies*

V. Lakshminarayanan *Electronic Circuit Design Ideas*

J. Lenk *Simplified Design of Linear Power Supplies*

M. Brown *Power Supply Cookbook*

B. Travis and I. Hickman *EDN Designer's Companion*

J. Dostal *Operational Amplifiers, Second Edition*

R. Marston *Electronics Circuits Pocketbook: Passive and Discrete Circuits*
(Vol. 2)

N. Dye and H. Granberg *Radio Frequency Transistors: Principles and Practical Applications*

Gates Energy Products *Rechargeable Batteries: Applications Handbook*

T. Williams *EMC for Product Designers*

J. Williams *Analog Circuit Design: Art, Science, and Personalities*

R. Pease *Troubleshooting Analog Circuits*

I. Hickman *Electronic Circuits, Systems and Standards*

R. Marston *Electronic Circuits Pocket Book: Linear ICs (Vol. 1)*

R. Marston *Integrated Circuit and Waveform Generator Handbook*

I. Sinclair *Passive Components: A User's Guide*

Simplified Design of Switching Power Supplies


John D. Lenk

Butterworth-Heinemann

Boston Oxford Melbourne Singapore Toronto Munich New Delhi Tokyo

Cover photograph courtesy of Linear Technology Corporation.

Copyright © 1995 by Butterworth-Heinemann

 A member of the Reed Elsevier group

All rights reserved.

No part of this publication may be reproduced, stored in a retrieval system, or transmitted, in any form or by any means, electronic, mechanical, photocopying, recording, or otherwise, without the prior written permission of the publisher.



Recognizing the importance of preserving what has been written, it is the policy of Butterworth-Heinemann to have the books it publishes printed on acid-free paper, and we exert our best efforts to that end.

Library of Congress Cataloging-in-Publication Data

Lenk, John D.

Simplified design of switching power supplies / by John D. Lenk.

p. cm.

Includes bibliographical references and index.

ISBN 0-7506-9507-2 (hardcover)

ISBN 0-7506-9821-7 (paperback)

1. Electronic apparatus and appliances—Power supply—Design and construction. 2. Switching power supplies—Design and construction. I. Title.

TK7868.P6L456 1995

621.381'044—dc20

94-32727

CIP

British Library Cataloguing-in-Publication Data

A catalogue record for this book is available from the British Library.

The publisher offers special discounts on bulk orders of this book.

For information, please contact:

Manager of Special Sales
Butterworth-Heinemann
313 Washington Street
Newton, MA 02158-1626
Tel: 617-928-2500
Fax: 617-928-2620

For information on all electronics publications available, contact our World Wide Web home page at: <http://www.bh.com/bh/>

10 9 8 7 6 5 4 3

Transferred to digital printing 2005

Greetings from the Villa Buttercup!
To my wonderful wife, Irene:
Thank you for being by my side all these years!

To my lovely family, Karen, Tom, Brandon, Justin, and Michael,
and to our Lambie and Suzzie: Be happy wherever you are!

And to my special readers: May good fortune find your doorway, bringing you good health and happy things. Thank you for buying my books!

To Frank Satlow, Karen Speerstra, Aliza Lamdan, John Fuller, the U.K. people, and the EDN people: A special thanks for making me an international best-seller, again (this is book number 81)!

Abundance!

This page intentionally left blank

Contents

Preface xiii

Acknowledgments xv

1 Switching Power-Supply Basics 1

- 1.1 Basic Switching-Regulator Functions 1
 - 1.1.1 Switching-Regulator Problems 2
 - 1.1.2 Switching-Duty Cycle 2
 - 1.1.3 Switching Frequency 2
 - 1.1.4 Transistor and Diode Characteristics 3
- 1.2 Typical Switching-Regulator Circuits 3
- 1.3 Switching-Regulator Theory 5
- 1.4 PWM versus PFM 7
- 1.5 Common Switching-Regulator Configurations 7
 - 1.5.1 Boost or Step-Up 8
 - 1.5.2 Continuous versus Discontinuous 10
 - 1.5.3 Buck-Boost or Inverting 11
 - 1.5.4 Buck or Step-Down 12
 - 1.5.5 Flyback 16
 - 1.5.6 Forward 21
 - 1.5.7 Current-Boosted Boost 21
 - 1.5.8 Current-Boosted Buck 22
 - 1.5.9 Cuk 22

2 Heat Sinks for Switching Power Supplies 25

- 2.1 Temperature-Related Design Problems 25
 - 2.1.1 Effects of Temperature on Transistor Collector Leakage 26
 - 2.1.2 Effects of Temperature on Transistor Current Gain 26

- 2.1.3 Effects of Temperature on Power Dissipation 26
- 2.1.4 Thermal Resistance 27
- 2.1.5 Thermal Runaway 27
- 2.1.6 Operating without Heat Sinks 28
- 2.1.7 Operating with Heat Sinks 29
- 2.1.8 Heat-Sink Ratings 29
- 2.1.9 Calculating Heat-Sink Capabilities 30
- 2.1.10 Practical Heat-Sink Considerations 31
- 2.1.11 Calculating Power Dissipation 32
- 2.2 Heat-Sink Mounting 33
 - 2.2.1 Interface Thermal-Resistance Values 34
 - 2.2.2 Fastening Techniques 34
 - 2.2.3 Preparation of Mounting Surface 36
 - 2.2.4 Thermal Compounds 38
- 2.3 Heat Sinks for ICs 38
 - 2.3.1 Working with Switching-Regulator ICs 40
 - 2.3.2 Maximum Power Dissipation 40
 - 2.3.3 Thermal Resistance for Switching-Regulator ICs 40
 - 2.3.4 Thermal Runaway in Regulator ICs 41
 - 2.3.5 Thermal and Excess-Current Shutdown 41
 - 2.3.6 IC Heat-Sink Calculations 41

3 Inductors/Transformers for Switching Power Supplies 43

- 3.1 Inductor Design Basics 43
 - 3.1.1 Choosing the Correct Inductance Value 44
 - 3.1.2 High-Inductance Problems 45
 - 3.1.3 Low-Inductance Problems 45
 - 3.1.4 Optimum Inductance 45
 - 3.1.5 Selecting Inductors for PWM Regulators 46
 - 3.1.6 Saturation Effects 46
 - 3.1.7 Air Gaps and Core Materials 48
 - 3.1.8 Core Material Trade-offs 48
 - 3.1.9 High-Flux MPP Cores 49
 - 3.1.10 DC Winding Resistance and I^2R Losses 50
 - 3.1.11 Temperature Rise 50
 - 3.1.12 High-Frequency Losses and Inductor Q 50
 - 3.1.13 EMI Problems 51
 - 3.1.14 Self-Resonant Frequency 52
- 3.2 Selecting the Inductor Value 52
 - 3.2.1 Inductor Value Basics 52
 - 3.2.2 Inductor Selection for Step-Up Regulators 53
 - 3.2.3 Inductor Selection for Step-Down Regulators 55
 - 3.2.4 Inductor Selection for Inverting Regulators 57
 - 3.2.5 Transformer Selection for Flyback Regulators 58

- 3.3 Inductor Catalogs, Data Sheets, and Kits 59
- 3.4 Designing Inductors and Transformers 59
 - 3.4.1 Simplified Inductor Design 59
 - 3.4.2 Simplified Transformer Design 71
 - 3.4.3 Example of Simplified Transformer Design 71

4 Testing and Troubleshooting 77

- 4.1 Basic Switching-Supply Tests 77
- 4.2 Basic Output Tests 78
- 4.3 Basic Load-Regulation Tests 80
- 4.4 Basic Line-Regulation Tests 81
- 4.5 Basic Efficiency Tests 81
- 4.6 Basic Ripple Tests 81
 - 4.6.1 Measuring Ripple with a Meter 82
 - 4.6.2 Measuring Ripple with a Scope 82
- 4.7 Measuring Transformer Characteristics 83
 - 4.7.1 Checking Transformer Polarity Markings 83
 - 4.7.2 Checking Transformer Impedance Ratio 84
 - 4.7.3 Checking Transformer Winding Balance 85
- 4.8 Basic Switching-Supply Troubleshooting 86
 - 4.8.1 Test-Measurement Techniques 86
 - 4.8.2 Electromagnetic Interference Suppression 87
- 4.9 Troubleshooting Hints 89

5 Simplified Design Approaches 95

- 5.1 Heat-Sink Design Approach 95
- 5.2 Micropower Switching Regulator 97
 - 5.2.1 Basic Design Approach 98
 - 5.2.2 Step-Up Design Approach 100
 - 5.2.3 Alternate Step-Up Design Approach 101
 - 5.2.4 Inductor Selection 101
 - 5.2.5 Low-Battery Detector 102
 - 5.2.6 Bias-Current Shutdown 102
 - 5.2.7 Typical Step-Up Application 103
 - 5.2.8 Bootstrap Operation 103
 - 5.2.9 Buck-Boost Application 104
 - 5.2.10 Step-Up Regulator with Voltage-Dependent Oscillator 104
 - 5.2.11 Feedback Compensation 106
 - 5.2.12 Short-Circuit Protection 106
 - 5.2.13 Power Supply with Positive and Negative Outputs 107
- 5.3 Inverting and Step-Down Switching Regulator 107
 - 5.3.1 Basic Design Approach 110
 - 5.3.2 Inverting Design Approach 111
 - 5.3.3 Step-Down Design Approach 112

5.3.4	Alternate Design Procedures	113
5.3.5	Inductor Selection	114
5.3.6	Low-Battery Detector	114
5.3.7	Device Shutdown	114
5.3.8	Feedback Compensation	115
5.3.9	Power-Transistor Interfaces	115
5.3.10	Inverting Medium-Power Interface	115
5.3.11	Inverting High-Power Interface	116
5.3.12	Step-Down Interface	117
5.3.13	Voltage-Dependent Oscillator	117
5.3.14	Short-Circuit Protection	118
5.4	Negative Switching Regulator (PWM)	119
5.4.1	Basic Design Approach	119
5.4.2	Negative-Input, Negative-Output Regulator	123
5.4.3	Dual-Output PBX Applications	123
5.4.4	Low-Power Switched-Capacitor Regulator	123
5.5	Switching Voltage Regulator	127
5.5.1	Step-Up Regulator Design	128
5.5.2	Step-Down Regulator Design	132
5.5.3	Inverting Regulator Design	136
5.5.4	Selection of Switching Components	141
5.5.5	Selection of Output-Filter Capacitors	142
5.5.6	EMI Problems	143
5.5.7	Simplified Design Equations	143
5.6	Low-Voltage Step-Up Converters	143
5.6.1	Basic Operating Principle	145
5.6.2	Pin Functions and Circuit Details	149
5.6.3	Low-Power Standby Mode	149
5.6.4	Power-Ready Output Pin	151
5.6.5	Start-up and Mode Considerations	151
5.6.6	Input Filtering	153
5.6.7	Output Filtering	153
5.6.8	Low-Battery Function	153
5.6.9	Shutdown Function	153
5.6.10	Inductor Selection	153
5.6.11	Simplified Inductor Selection	156
5.6.12	Capacitor Selection	157
5.6.13	Selecting Low-Power Switching Diodes	157
5.6.14	Rectifier Selection (High Power)	157
5.6.15	Output Current versus Input Voltage	158
5.7	Super Voltage Converter (Charge Pump)	160
5.7.1	Basic Operating Principle	161
5.7.2	Theoretical Power-Efficiency Considerations	162
5.7.3	Do's and Don'ts	163
5.7.4	Basic Negative Voltage Converter	164

5.7.5	Output Ripple	164
5.7.6	Paralleling Devices	164
5.7.7	Cascading Devices	167
5.7.8	Changing Oscillator Frequency	167
5.7.9	Positive Voltage Doubling	169
5.7.10	Combined Positive and Negative Outputs	169
5.7.11	Voltage Splitting	170
5.7.12	Regulated Negative Supply Voltage	170
5.8	Charge Pump with Shutdown	171
5.9	Tabular Design of Switching Regulator	171
5.9.1	Low-Power Step-Up Converters	172
5.9.2	Medium-Power Step-Up Converters	173
5.9.3	Low-Power Step-Down Converters	174
5.9.4	Low-Power Inverters	174
5.9.5	Medium-Power Inverters	174
5.10	Tabular Design of Hybrid Switching Regulators	175
5.10.1	Basic Design Procedure	176
5.10.2	Input Voltage Requirements	181
5.10.3	Output Voltage Adjustment	181
5.10.4	Capacitor and Inductance Selection	181
5.10.5	Heat-Sink Calculations	182
5.10.6	Approximating Device Power	183
5.10.7	Wiring Considerations	183
5.11	Switching Regulator	183
5.11.1	Block Diagram Description	184
5.11.2	V_{IN} Pin	189
5.11.3	Ground Pin	189
5.11.4	Feedback Pin	190
5.11.5	V_C Pin and Error Amplifier	191
5.11.6	Power Dissipation	192
5.11.7	Positive-to-Negative Converter (Inverter)	193
5.11.8	Negative-Boost Converter	196
5.11.9	Inductor Selection	199
5.11.10	Micropower Shutdown and Undervoltage Lockout	207
5.11.11	Five-Pin Current Limit	207
5.11.12	Soft Start	209
5.11.13	Output Filters	211
5.11.14	Output Overshoot	213

For Further Information 215

Index 217

This page intentionally left blank